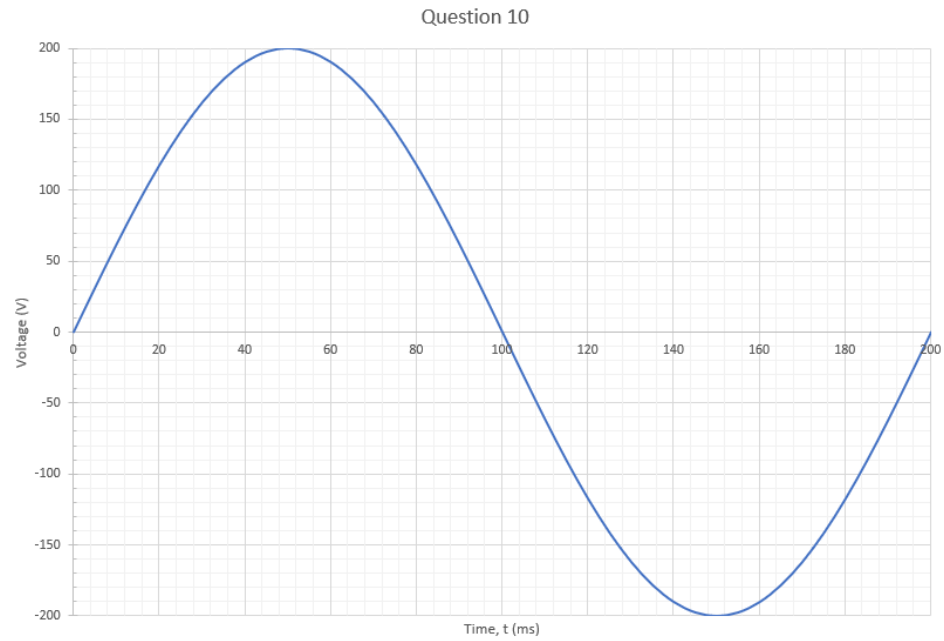


Skyler MacDougall

Homework 1: Due 1/22/2020

10.

1. Draw a waveshape of a sinusoidal voltage having a peak value of 200V and a frequency of 5Hz.



2. If the voltage is zero at $t = 0$, what is the voltage at $t = 5ms$? $75ms$? $150ms$?

Time (t, ms)	Voltage (V)
5	≈ 31
75	≈ 141
150	-200

11. A sinusoidal current has an effective value of 50A. Calculate the peak value of current.

$$50A * \frac{\sqrt{2}}{2} \approx 35A \quad (1)$$

12. A sinusoidal voltage of 120V is applied to a 10Ω resistor. Calculate

1. the effective current through the resistor.

$$\frac{120V}{10\Omega} = 12A \quad (2)$$

2. the peak voltage across the resistor.

$$120V * \sqrt{2} \approx 170V_{RMS} \quad (3)$$

3. the power dissipated by the resistor.

$$120V * 12A = 1440W \quad (4)$$

4. The peak power dissipated by the resistor.

$$170V_{RMS} * (12A * \sqrt{2}) = 2880W \quad (5)$$


13. A distorted voltage contains an 11th harmonic of 20V, 253Hz. Calculate the frequency of the fundamental.

$$253Hz * 11^{th} Harmonic \approx 2.6kHz \quad (6)$$

14. The current in a 60Hz single phase motor lags 36 degrees behind the voltage. Calculate the time interval between positive peaks of voltage and current.

$$\frac{1}{60Hz} * \frac{360^\circ - 36^\circ}{360^\circ} = \frac{1}{6} seconds = 0.166 seconds \quad (7)$$

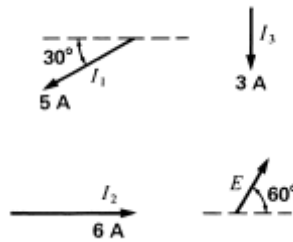15. Determine the phase angle between the following phasors and, in each case, indicate which phasor is lagging.



1. I_1 and I_3

$$\begin{aligned} \angle I_1 - \angle I_3 &= -60^\circ \\ \therefore \\ I_1 \text{ lags } I_3 \text{ by } 60^\circ \end{aligned} \quad (8)$$

2. I_2 and I_3


$$\begin{aligned} \angle I_2 - \angle I_3 &= -90^\circ \\ \therefore \\ I_2 \text{ lags } I_3 \text{ by } 90^\circ \end{aligned} \quad (9)$$

3. E and I_1


$$\begin{aligned} \angle E - \angle I_1 &= -150^\circ \\ \therefore \\ E \text{ lags } I_1 \text{ by } 150^\circ \end{aligned} \quad (10)$$

16. The voltage applied to an AC magnet is given by the expression $E = 160\sin\phi$, and the current is $I = 20\sin(\phi - 60^\circ)$, all angles being expressed in degrees.

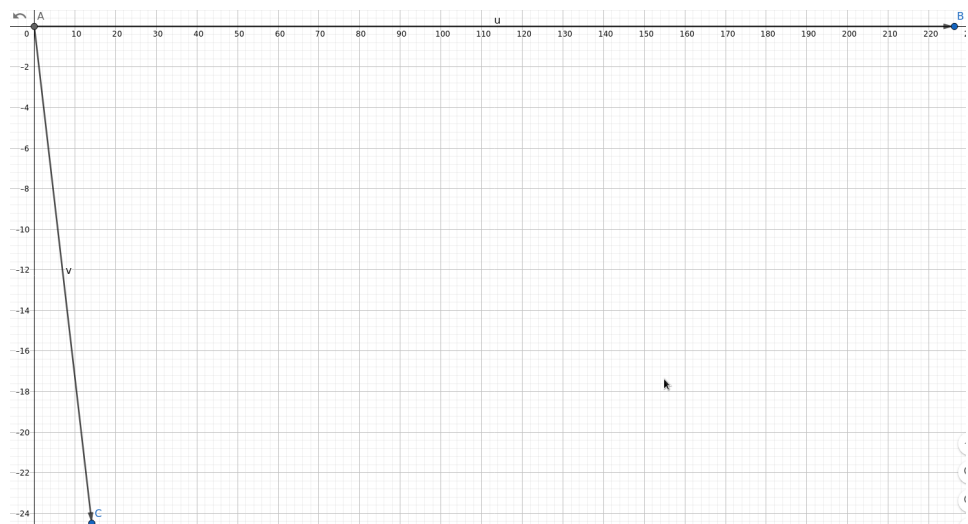1. Draw the phasor diagram for E and I , using effective values.



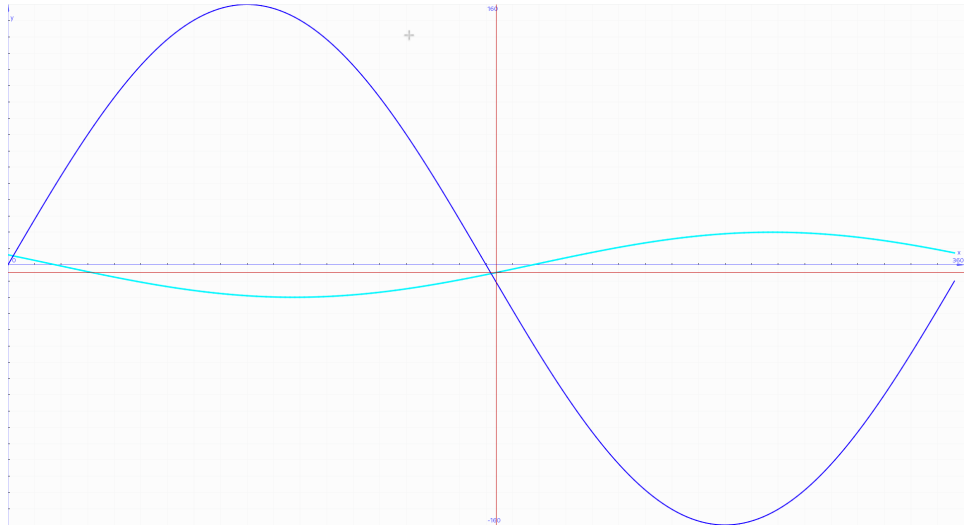2. Draw the waveshape of E and I as a function of ϕ .



3. Calculate the peak positive power and the peak negative power in the circuit.