

# Skyler MacDougall

## Homework 10: due 3/30/2020

2. A wye-connected squirrel-cage motor having a synchronous speed of 900r/min has a stator resistance of  $0.7\Omega$  and an equivalent rotor resistance of  $0.5\Omega$ . If the total leakage reactance is  $5\Omega$  and the line-to-neutral voltage is 346V, calculate the following:


1. The value of  $Z_1$  and the angle  $\alpha$

$$\begin{aligned} Z_1 &= \sqrt{R_1^2 + x^2} = \sqrt{0.7^2 + 5^2} \\ Z_1 &= 5.048\Omega \\ \alpha &= \tan^{-1}\left(\frac{X}{R_1}\right) = \tan^{-1}\left(\frac{5\Omega}{0.7\Omega}\right) \\ \alpha &= 82.03^\circ \end{aligned} \quad (1)$$

2. The speed when the breakdown torque is reached

$$\begin{aligned} n_b &= n_s \left(1 - \left(\frac{R_2}{Z_1}\right)\right) = 900 \left(1 - \left(\frac{0.5\Omega}{5.048\Omega}\right)\right) \\ |n_b &= 810.85| \end{aligned} \quad (2)$$

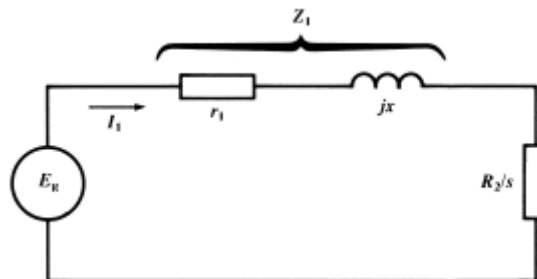3. the current  $I_1$  at the breakdown torque (see below)




$$\begin{aligned} I_1 &= \frac{E_L}{2Z_1 \cos(\frac{\alpha}{2})} = \frac{346V}{2 * 5.048 * \cos(\frac{82.03^\circ}{2})} \\ |I_1 &= 45.419A| \end{aligned} \quad (3)$$

4. The value of the breakdown torque [N\*m]

$$\begin{aligned} T_b &= \frac{9.55(I_1^2 Z_1)}{n_s} = \frac{9.55(45.419A^2 * 5.048\Omega)}{900r/min} \\ |T_b &= 110.498N * m| \end{aligned} \quad (4)$$

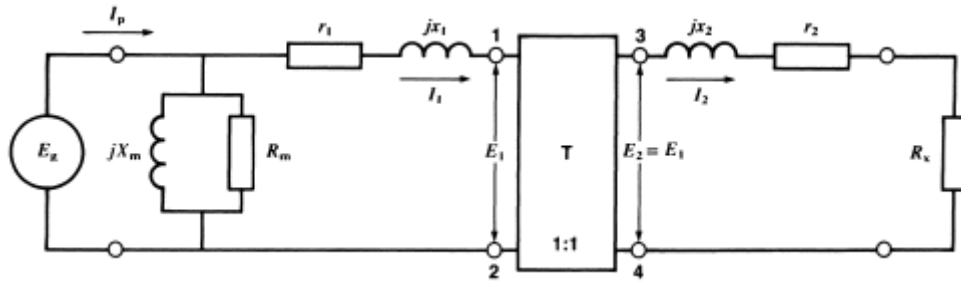4. A 550V, 1780r/min, 3-phase, 60Hz, squirrel cage induction motor running at no-load draws a current of 12A and a total power of 1500W. Calculate the value of  $X_m$  and  $R_m$  per phase.



$$S = VA = 550V * 12A = 6.6kVA \quad (5)$$


$$Q = \sqrt{6.6kVA^2 - 1.5kW^2} = 6.4kVAR$$

$$R = \frac{V}{P} = \frac{550V}{1500W}$$

$$X = \frac{V}{Q} = \frac{550V}{6.4kVAR}$$

$$\boxed{R = 0.36\Omega; X = 0.09\Omega}$$

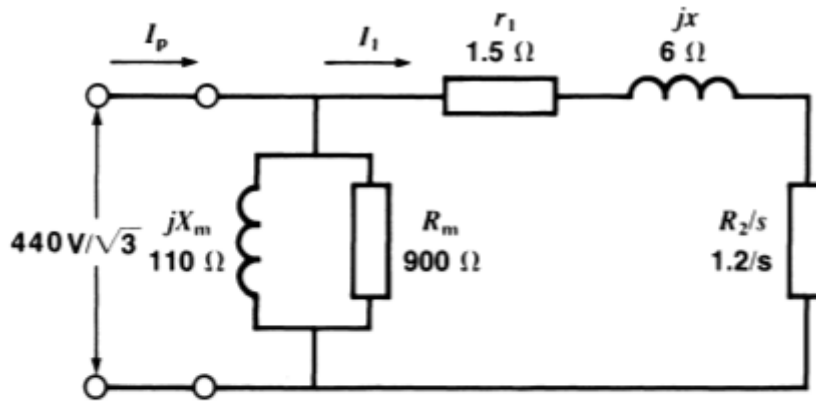9. Consider the 5hp motor whose equivalent circuit shown below.



#### Motor rating:

5 hp, 60 Hz, 1800 r/min, 440 V, 3-phase  
 full-load current: 7 A  
 locked-rotor current: 39 A

$r_1$  = stator resistance  $1.5 \Omega$

$r_2$  = rotor resistance  $1.2 \Omega$

$jx$  = total leakage reactance  $6 \Omega$

$jX_m$  = magnetizing reactance  $110 \Omega$

$R_m$  = no-load losses resistance  $900 \Omega$

The no-load losses include the iron losses plus windage and friction losses.

#### Figure 12

Equivalent circuit of a 5 hp, squirrel-cage induction motor. Because there is no external resistor in the rotor,  $R_2 = r_2$ .

1. Calculate the values of the inductances (in mH) of the leakage and magnetizing reactances.

$$L_m = \frac{X}{2\pi f} = \frac{110\Omega}{2\pi(60Hz)} \quad (6)$$

$$L_x = \frac{X}{2\pi f} = \frac{6\Omega}{2\pi(60Hz)}$$

$$\boxed{L_x = 15.9mH; L_m = 291.8mH}$$

2. Determine the values of the leakage reactance and magnetizing reactance at a frequency of 50Hz.

$$X_m = L_m * 2\pi f = 15.9mH * 2\pi * 50Hz \quad (7)$$

$$X_m = L_m * 2\pi f = 291.8mH * 2\pi * 50Hz$$

$$\boxed{X = 5\Omega; X_m = 91.6\Omega}$$


3. Calculate the 50Hz line to neutral voltage to obtain the same magnetizing current and compare it with the voltage at 60Hz.

$$V' = V * \frac{f_2}{f_1} = \frac{440}{\sqrt{3}} V * \frac{50Hz}{60Hz} \quad (8)$$

$$V' \approx 212V$$

10. The 5hp motor represented by the equivalent circuit of the image above is connected to a 503V(line-to-line), 3-phase, 80Hz source. The stator and rotor resistances are assumed to remain the same.

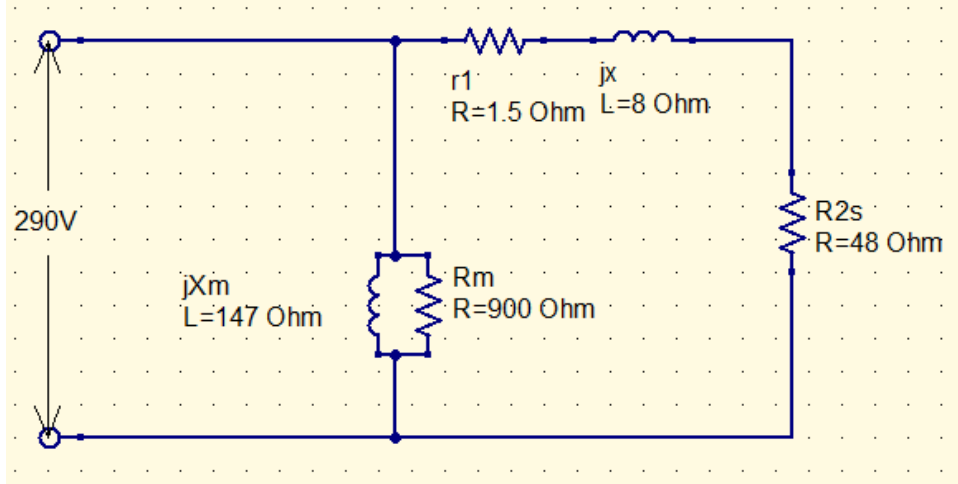1. Determine the equivalent circuit when the motor runs at 2340r/min.



2. Calculate the value of the torque [N\*m] and the power [hp] developed by the motor.

$$P_r = \left( \frac{V}{\sqrt{X^2 + R_1^2}} \right)^2 * R_2/s * phases \quad (9)$$

$$P_r = \left( \frac{290V}{\sqrt{8\Omega^2 + (1.5\Omega + 48\Omega)^2}} \right)^2 * R_2/s * 3 phases$$

$$P_r = \left( \frac{290V}{50.14\Omega} \right)^2 * \frac{1.2}{0.025} * 3 phases$$

$$P_r = (5.78A)^2 * 48\Omega * 3 phases$$

$$P_r = 3819.39(A^2) * 144\Omega$$

$$T = 9.55 \frac{4817W}{2400rpm}$$

$$P = \frac{nT}{9.55} = \frac{2340rpm * 19.2Nm}{9.55} = 4696W$$

$$\boxed{T = 19.2Nm; P_r = 6.29hp}$$

$$s = \frac{n_s - n}{n_s} \quad (10)$$

$$s * n_s = n_s - n$$