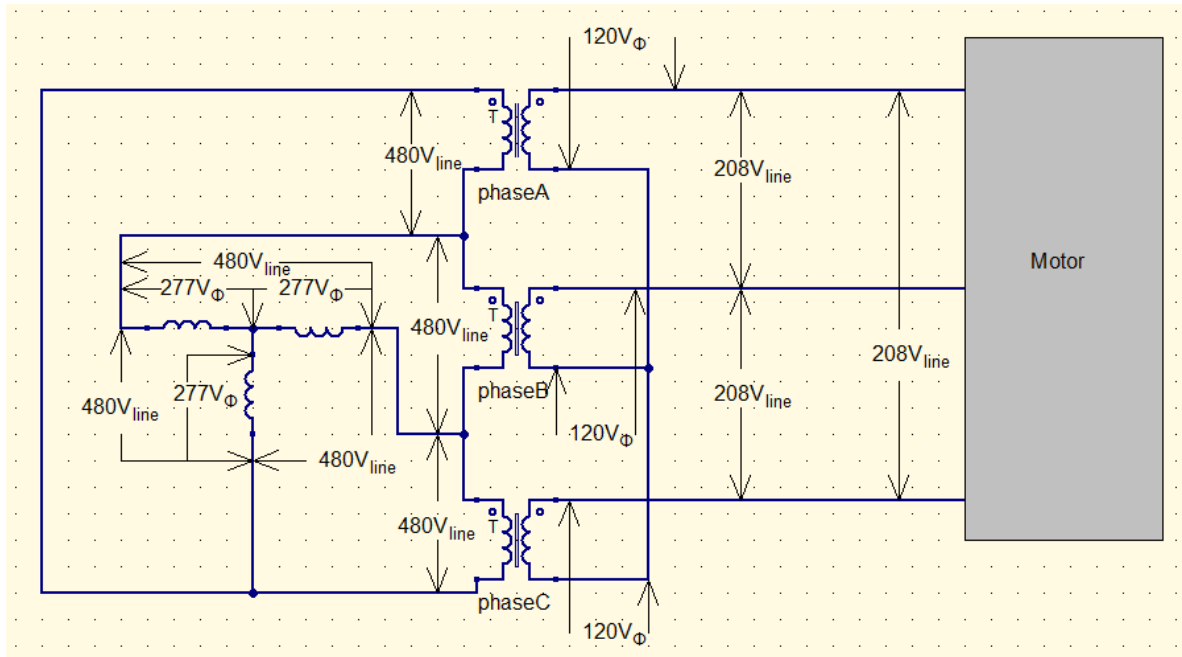


1. Clearly label each voltage.



2. What is the synchronous speed of this motor?

$$n_s = 120 * \frac{f}{p} = 120 * \frac{60Hz}{6poles} \quad (1)$$

$$\underline{n_s = 1200rpm}$$

3. How many poles does this motor have?

$$poles = phases * 2 = 3 * 2 \quad (2)$$

$$\underline{6 poles}$$

4. What is the slip of this motor?

$$s = \frac{n_s - n}{n_s} = \frac{1200rpm - 1076rpm}{1200rpm} \quad (3)$$

$$\underline{s = 0.103}$$

5. What is the mechanical output in BHP (brake horsepower) of this motor at full speed?

$$rated\ hp * efficiency = 10hp * 0.8 \quad (4)$$

$$\underline{8BHP}$$

6. What is the total impedance Z_{motor} of this motor at full load?

$$Z = \frac{V}{FLA} = \frac{208V}{30A} = 6.93\bar{\Omega} \quad (5)$$

$$\theta = \cos^{-1}(pf) = \cos^{-1}(0.7071) \approx \cos^{-1}\left(\frac{\sqrt{2}}{2}\right) = 45^\circ$$

$$\underline{Z = 6.93\bar{\Omega} < 45^\circ}$$

7. What is the resistive impedance R_{motor} of this motor at full load?

$$|Z| * \cos(\theta) = \frac{\sqrt{2}}{2} \quad (6)$$

$$R = 4.9\Omega$$

8. What is the reactive impedance X_{motor} of this motor at full load?

$$|Z| * \sin(\theta) = 6.93 * \frac{\sqrt{2}}{2} \quad (7)$$

$$X = 4.9\Omega$$

9. What is the $\frac{X}{R}$ ratio of the motor?

10. What is the full load apparent power drawn by this motor?

$$S = FLA * V * \sqrt{3} = 208V * 30A * \sqrt{3} \quad (8)$$

$$S = 10.8kVA$$

11. What is the Full Load Active power drawn by this motor?

$$P = S * \cos(\theta) = 10.8kVA * \frac{\sqrt{2}}{2} \quad (9)$$

$$\underline{|P = 7.63668kW|}$$

12. What is the full load reactive power drawn by this motor?

$$Q = S * \sin(\theta) = 10.8kVA * \frac{\sqrt{2}}{2} \quad (10)$$

$$\underline{|Q = 7.63668kW|}$$

13. What is the locked rotor apparent power drawn by the motor?

$$S = V * LRA * \sqrt{3} = 208V * 180A * \sqrt{3} \quad (11)$$

$$\underline{|S = 64.8kVA|}$$

14. Determine $I_{secondary_{line}}$.

$$I = \frac{S}{V} = \frac{10.8kVA}{208V} \quad (12)$$

$$\underline{|I = 51.96A|}$$

15. Determine $I_{secondary_{\phi}}$.

$$I_{line} = I_{\phi} = 51.96A \quad (13)$$

16. Determine $I_{primary_\phi}$.

$$I_{primary} = \frac{I_{secondary}}{a} = \frac{51.96A}{4} \quad (14)$$
$$\underline{\underline{|I_{primary_\phi} = 13A|}}$$

17. Determine $I_{primary_{line}}$.

$$I_{line} = I_\phi * \sqrt{3} = 13A * \sqrt{3} \quad (15)$$
$$\underline{\underline{|I_{line} = 22.5A|}}$$

18. Determine $I_{utility_{line}}$.

$$I_{utility} = I_{primary} = 22.5A \quad (16)$$

19. Determine $P_{secondary_\phi}$.

$$P = VI = 120V * 51.96A = 6.235kW \quad (17)$$

20. Determine $P_{secondary_{3\phi}}$

$$P_{3\phi} = 3 * P = 3 * 6.235kW = 18.7kW \quad (18)$$

21. Determine $P_{primary_\phi}$.

$$P = VI = 480V * 13A = 6.24kW \quad (19)$$

22. Determine $P_{primary_{3\phi}}$

$$P_{3\phi} = 3 * P = 3 * 6.24kW = 18.7kW \quad (20)$$

23. Determine $P_{utility}$.

$$P_{utility} = P_{primary_{3\phi}} = 18.7kW \quad (21)$$