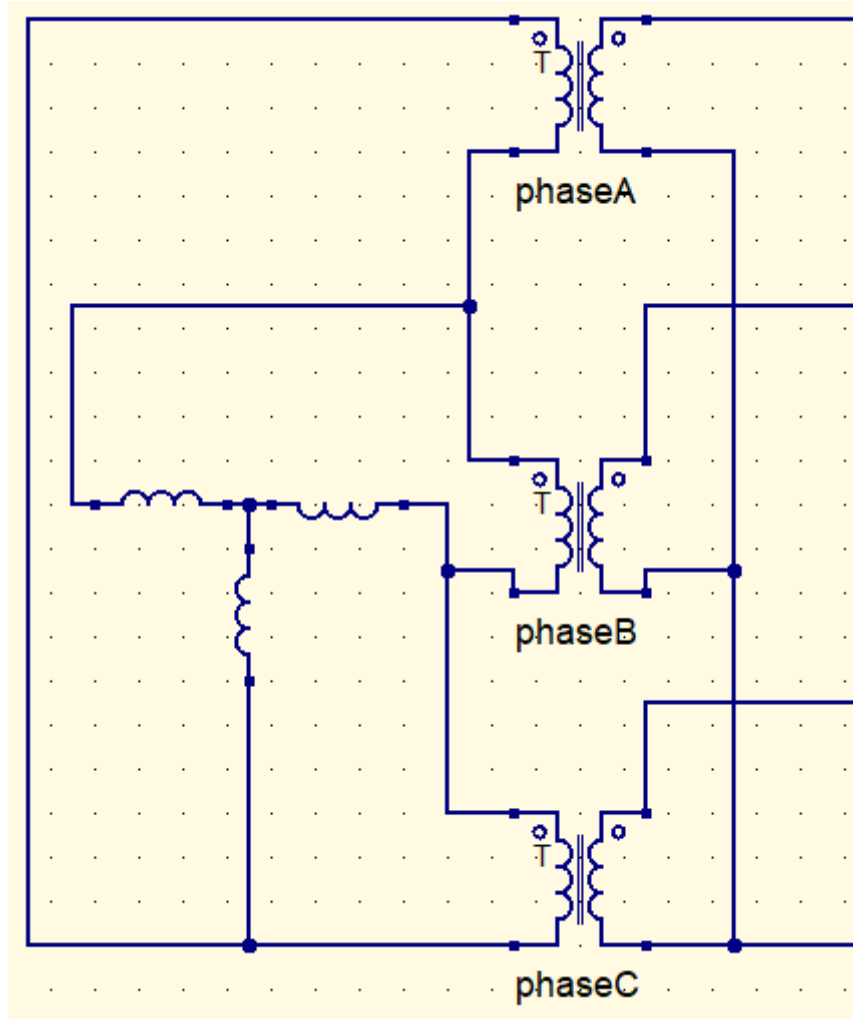


1. Draw the circuit of a 3-phase 4160/2400V generator.


Note that the generator is in a WYE configured generator. Ignore any generator impedance. Draw this first before moving on.

Connect the generator to the primary of a 3-phase transformer. You will only have 3 lines from the generator to the transformer primary. The transformer is rated at 1000kVA, 4160-208/120V, 60Hz. In this step, there is no load on the transformer, the secondary of the transformer is open-circuited.




2. Clearly label and determine of the following:

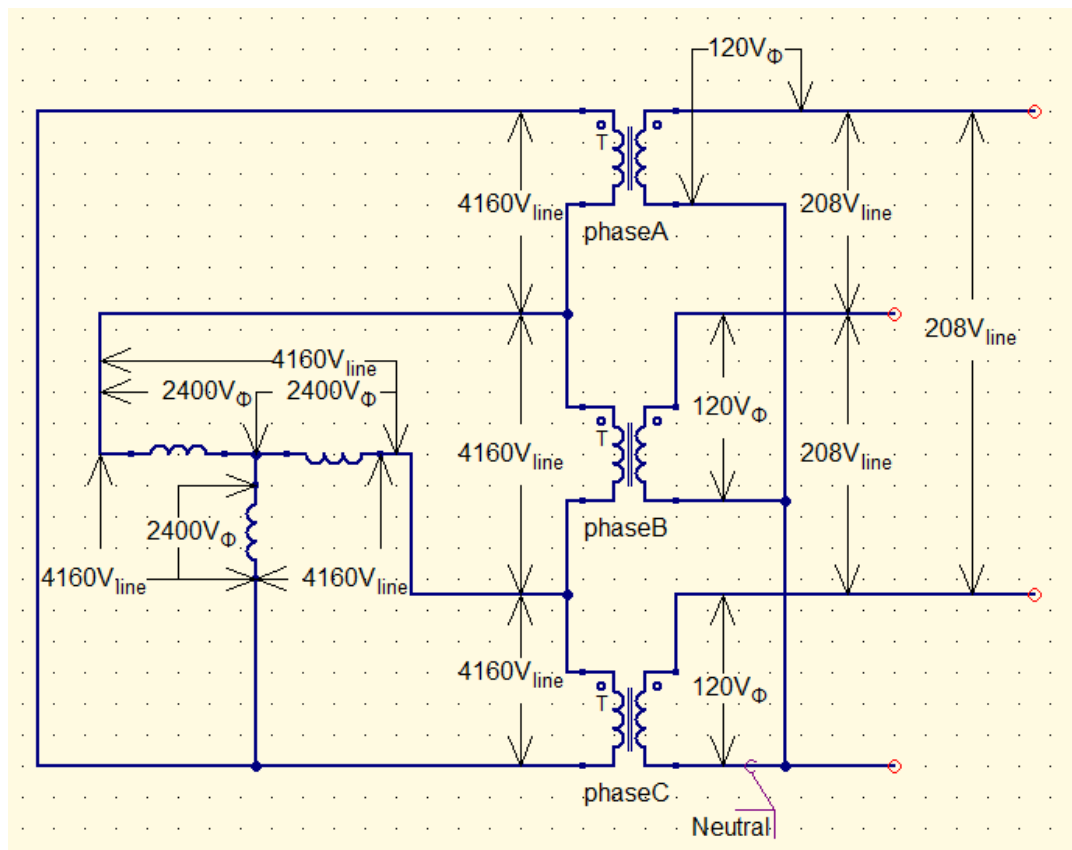1.  $V_{generator\phi}$
2.  $V_{generator_{line}}$
3.  $V_{primary\phi}$
4.  $V_{primary_{line}}$
5.  $V_{secondary\phi}$
6.  $V_{secondary_{line}}$



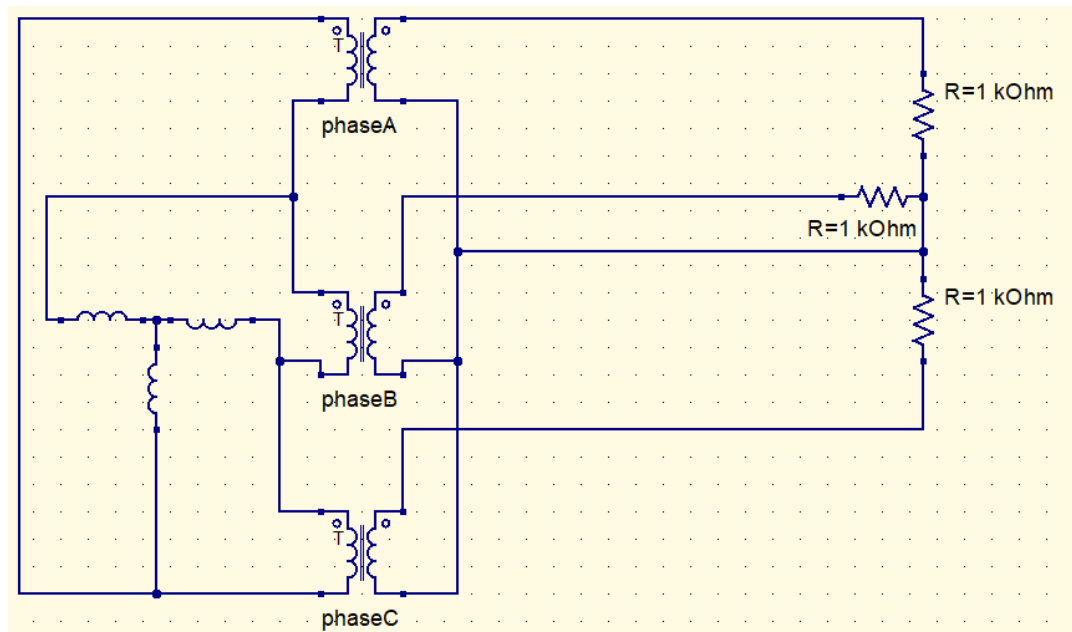3. Connect a  $1k\Omega$  resistor across each phase of the secondary of the transformer to neutral. Redraw the circuit.



4.

1. Determine  $V_{load}$  across each resistor. Show this voltage in the circuit diagram.

$$V_{\phi} = 120V = V_a \rightarrow V_{neutral} = V_b \rightarrow V_{neutral} = V_c \rightarrow V_{neutral} \quad (1)$$

$$\vdots$$

$$V_{load} = 120V$$

2. Find  $I_{load}$  through each resistor.

$$I_{load} = \frac{V_{load}}{R} = \frac{120V}{1k\Omega} = 120mA \quad (2)$$

3. Determine the current for each line from each of the secondary of the transformer to the load  $I_{secondary_{line}}$  .

$$\begin{aligned} I_{load} &= I_{secondary_{line}} \\ \therefore \\ I_{secondary_{line}} &= 120mA \end{aligned} \quad (3)$$

4. Determine  $I_{secondary_{\phi}}$  .

$$\begin{aligned} &WYE \text{ config} \\ \therefore \\ I_{secondary_{\phi}} &= 120mA \end{aligned} \quad (4)$$

5. Determine  $I_{primary_{\phi}}$  .

$$\begin{aligned} I_{primary_{\phi}} &= \frac{I_{secondary_{\phi}}}{a}; a = 34.6 \\ I_{primary_{\phi}} &= \frac{120mA}{34.6} \approx 3.5mA \end{aligned} \quad (5)$$

6. Determine  $I_{primary_{line}}$  .

$$\begin{aligned} I_{primary_{line}} &= I_{primary_{\phi}} * \sqrt{3} \\ I_{primary_{line}} &= 5.996mA \approx 6mA \end{aligned} \quad (6)$$

7. Determine  $I_{generator_{line}}$  .


$$\begin{aligned} I_{generator_{line}} &= I_{primary_{line}} \\ \therefore \\ I_{generator_{line}} &\approx 6mA \end{aligned} \quad (7)$$

8. Determine  $I_{generator_{\phi}}$  .

$$I_{generator_\phi} = I_{primary_\phi} \quad (8)$$

$$\vdots$$

$$I_{generator_\phi} \approx 3.5mA$$

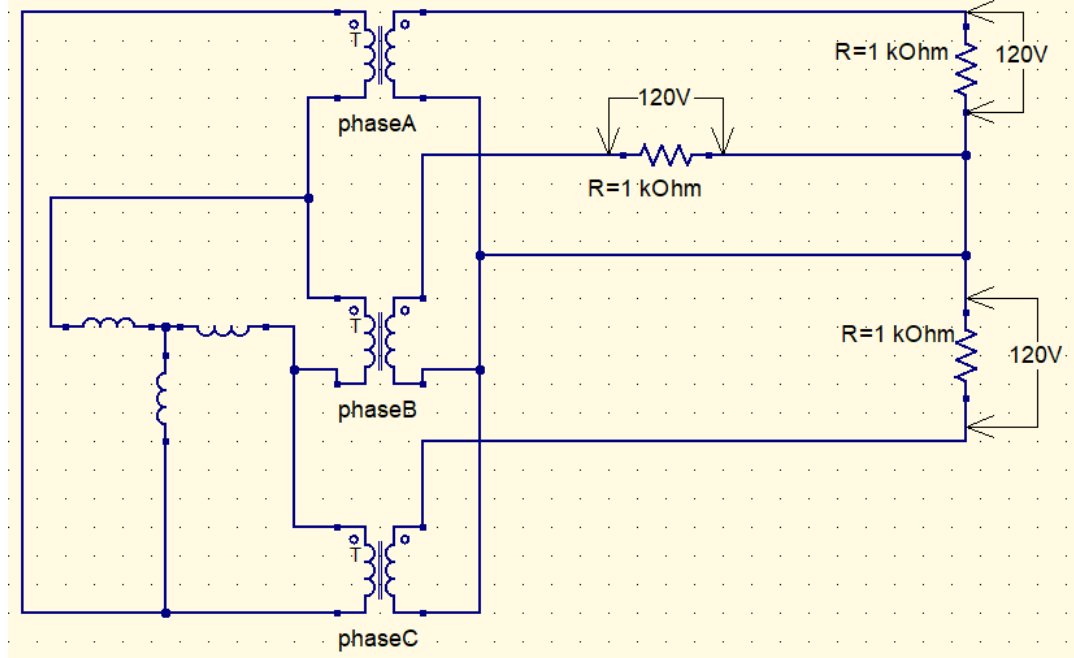

5. From the numbers above, determine:

$$1. P_{generator_\phi}$$

$$P_\phi = I_\phi V_\phi \quad (9)$$

$$P_{generator_\phi} = 3.5mA * 4160V$$

$$P_{generator_\phi} = 14.4W$$

$$2. P_{generator_{3\phi}}$$

$$P_{3\phi} = 3P_\phi \quad (10)$$

$$P_{generator_{3\phi}} = 14.4W * 3$$

$$P_{generator_{3\phi}} \approx 43W$$

$$3. P_{primary_\phi}$$

$$P_\phi = I_\phi V_\phi \quad (11)$$

$$P_{primary_\phi} = 3.5mA * 4160V$$

$$P_{primary_\phi} = 14.4W$$

4.  $P_{primary_{3\phi}}$

$$\begin{aligned} P_{3\phi} &= 3P_{\phi} \\ P_{primary_{3\phi}} &= 14.4W * 3 \\ P_{primary_{3\phi}} &\approx 43W \end{aligned} \tag{12}$$

5.  $P_{secondary_{\phi}}$

$$\begin{aligned} P_{\phi} &= I_{\phi} V_{\phi} \\ P_{secondary_{\phi}} &= 120mA * 120V \\ P_{secondary_{\phi}} &= 14.4W \end{aligned} \tag{13}$$

6.  $P_{secondary_{3\phi}}$

$$\begin{aligned} P_{3\phi} &= 3P_{\phi} \\ P_{secondary_{3\phi}} &= 14.4W * 3 \\ P_{secondary_{3\phi}} &\approx 43W \end{aligned} \tag{14}$$

7.  $P_{load_{\phi}}$

$$\begin{aligned} P_{\phi} &= I_{\phi} V_{\phi} \\ P_{load_{\phi}} &= 120mA * 120V \\ P_{load_{\phi}} &= 14.4W \end{aligned} \tag{15}$$

8.  $P_{load_{3\phi}}$

$$\begin{aligned} P_{3\phi} &= 3P_{\phi} \\ P_{secondary_{3\phi}} &= 14.4W * 3 \\ P_{secondary_{3\phi}} &\approx 43W \end{aligned} \tag{17}$$