

Homework 1b

EEET-427-01:Controls Systems


Blizzard MacDougall

09/27/2021

For each problem:

1. Find the differential equation that relates V_{out} to V_{in} .
2. Rewrite the differential equation in Laplace form.
3. Make an unreduced block diagram.
4. Reduce the block diagram into a single block.
5. Find the transfer function of the system.
6. Find the DC gain of the transfer function.
7. Find the time constant of the circuit.

1 Problem 1

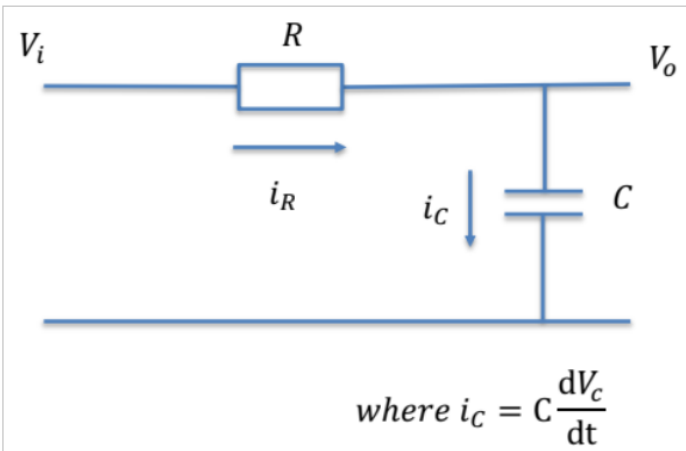

1)

$$\begin{aligned} i_R &= i_C \\ \frac{v_R}{R} &= C \frac{dv_C}{dt} \\ v_R &= v_i - v_o; \quad v_C = v_o \\ \frac{v_i - v_o}{R} &= C \frac{dv_o}{dt} \\ \frac{1}{RC}(v_i) &= \frac{dv_o}{dt} + \frac{1}{RC}(v_o) \end{aligned} \tag{1}$$

2)

$$\frac{1}{RC}V_i = sV_o + \frac{1}{RC}V_o \quad (2)$$

3) .

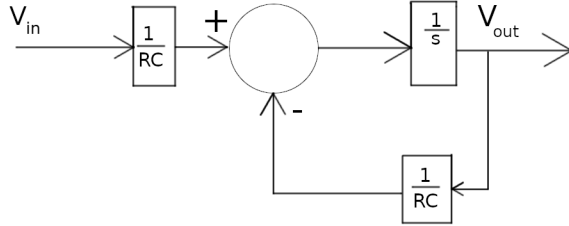


Figure 1: Problem 1 Unreduced Block Diagram

4) .

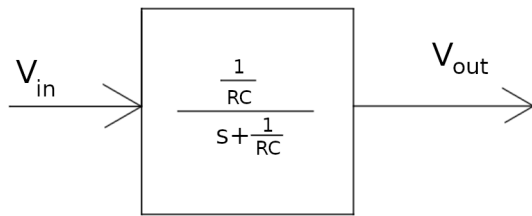


Figure 2: Problem 1 Reduced Block Diagram

5)


$$\frac{V_o}{V_i} = \frac{\frac{1}{RC}}{s + \frac{1}{RC}} \quad (3)$$

6) DC gain = 1

7)

$$\tau = RC \quad (4)$$

2 Problem 2

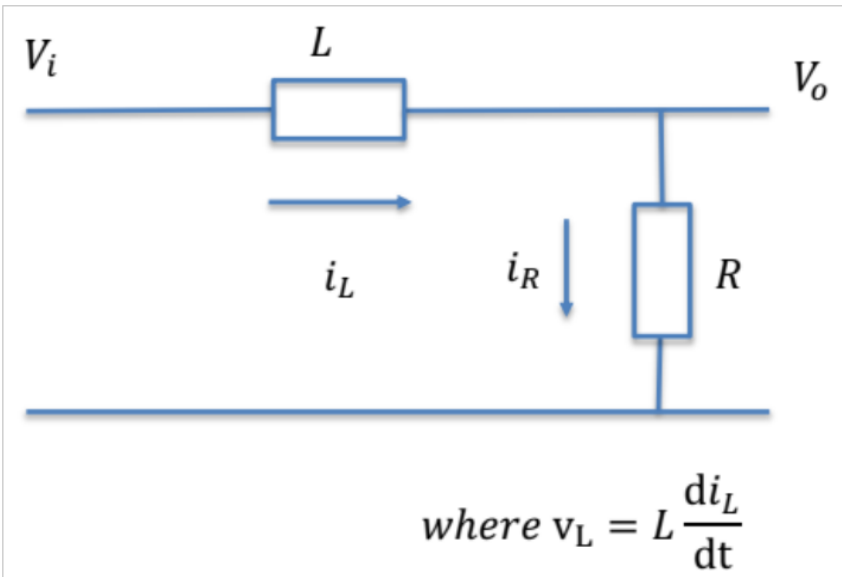

1)

$$\begin{aligned} i_R &= \frac{v_i - v_o}{R} = i_L \\ v_L &= L \frac{di_L}{dt} = v_o \end{aligned} \quad (5)$$

2)

$$\frac{1}{RC} V_i = sV_o + \frac{1}{RC} V_o \quad (6)$$

3) .

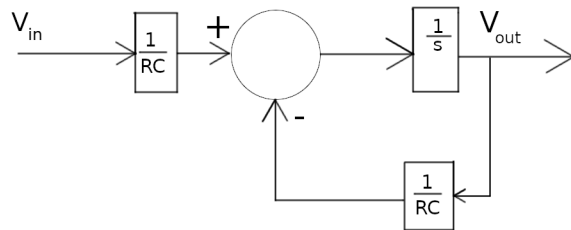


Figure 3: Problem 1 Unreduced Block Diagram

4) .

5)

$$\frac{V_o}{V_i} = \frac{\frac{1}{RC}}{s + \frac{1}{RC}} \quad (7)$$

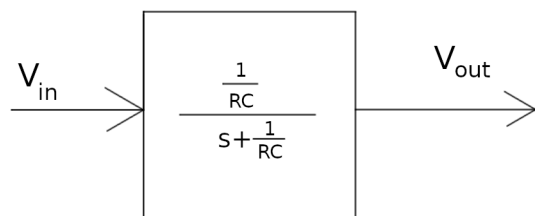


Figure 4: Problem 1 Reduced Block Diagram

6) DC gain = 1

7)

$$\tau = RC \quad (8)$$